

## Ohms law, Current, voltage, Power and energy

1. An electric current of 10 A is the same as \_\_\_\_\_
- a) 10 J/C
  - b) 10 V/C
  - c) 10C/sec
  - d) 10 W/sec
- 

*Ans C*

2. Consider a circuit with two unequal resistances in parallel, then \_\_\_\_\_
- a) large current flows in large resistor
  - b) current is same in both
  - c) potential difference across each is same
  - d) smaller resistance has smaller conductance
- 

*Ans C*

3. In which of the following cases is Ohm's law not applicable?
- a) Electrolytes
  - b) Arc lamps
  - c) Insulators
  - d) AC bridges
- 

*Ans C*

4. Which of the following bulbs will have high resistance?
- a) 220V, 60W
  - b) 220V, 100W
  - c) 115V, 60W
  - d) 115V, 100 W
- 

*Ans a*

5. Ohm's law is not applicable to \_\_\_\_\_
- a) dc circuits
  - b) high currents
  - c) small resistors
  - d) semi-conductors
- 

*Ans d*

6. Conductance is expressed in terms of \_\_\_\_\_
- a) mho
  - b) mho/m
  - c) ohm/m
  - d) m/ohm
- 

*Ans a*

7. In a current-voltage relationship graph of a linear resistor, the slope of the graph will indicate \_\_\_\_\_
- a) conductance



- b) resistance
  - c) resistivity
  - d) a constant
- 

*Ans b*

8. Which of the following type of circuits in electrical engineering cannot be analyzed using Ohm's law?
- a) Unilateral
  - b) Bilateral
  - c) Linear
  - d) Conductors
- 

*Ans a*

9. When a bulb uses 0.25A from a 24V battery source, what is its Resistance (R) ?
- a)  $50\Omega$
  - b)  $96\Omega$
  - c)  $95\Omega$
  - d)  $72\Omega$
- 

*Ans*

10. The Tungsten filament in a light bulb has a resistance of-
- a) Linear
  - b) Non-Linear
  - c) Fixed
  - d) a & b are correct
- 

*Answer- B*

11. Open circuit resistance is
- a) low
  - b) Infinitely High
  - c) Zero
  - d) a & b are correct
- 

*Ans b*

12. Short circuit resistance is
- a) low
  - b) Infinitely High
  - c) Zero
  - d) a & b are correct
- 

*Ans C*

13. A kilowatt-hour (kWh) is a big unit of \_\_\_\_\_ electricity.
- a) work
  - b) energy
  - c) conductance
  - d) power



---

Answer- B

14. In a conductor, if 6-coulomb charge flows for 2 seconds. The value of electric current will be
- a) 3 ampere
  - b) 3 volts
  - c) 2 amperes
  - d) 2 volts
- 

Ans a

15. Which of the following elements of electrical engineering cannot be analyzed using Ohm's law?
- a) Capacitors
  - b) Inductors
  - c) Transistors
  - d) Resistance
- 

Ans C

16. Which of the following is correct about the power consumed by  $R_1$  and  $R_2$  connected in series if the value of  $R_1$  is greater than  $R_2$ ?
- a)  $R_1$  will consume more power
  - b)  $R_2$  will consume more power
  - c)  $R_1$  and  $R_2$  will consume the same power
  - d) The relationship between the power consumed cannot be established
- 

Ans a,

*$P = I^2 \cdot R$ . When two resistors are connected in series the current flowing through the resistors is the same and thus, power consumed by the larger resistor will be more.*

---

17. What kind of quantity is an Electric potential?
- a) Vector quantity
  - b) Tensor quantity
  - c) Scalar quantity
  - d) Dimensionless quantity
- 

Answer: c

*Explanation: Electric potential refers to the work done to bring a unit positive charge from a point with higher potential to a point with lower potential. Since electric potential only has magnitude but no direction, it is a scalar quantity.*

---

## Series and Parallel circuit

1. A certain circuit is composed of two parallel resistors. The total resistance is  $1,403 \Omega$ . One of the resistors is  $2 \Omega$ . The other resistor value is

- a)  $1,403 \Omega$
- b)  $4.7 \text{ k}\Omega$
- c)  $2 \text{ k}\Omega$
- d)  $3,403 \Omega$



---

*Answer: (b) 4.7 k $\Omega$*

Q2: A voltage divider consists of two 100 k $\Omega$  resistors and a 12 V source. What will the voltage be if a load resistor of 1 M $\Omega$  is connected to the output?

- a) 0.57 V
- b) 6 V
- c) 12 V
- d) 5.7 V

---

*Answer: (d) 5.7 V*

3: A Voltage divider consists of two 68 k $\Omega$  resistors and a 24 V source. The voltage across one of the resistor is

- a) 12 V
- b) 24 V
- c) 0 V
- d) 6 V

---

*Answer: (a) 12 V*

4: Two 3.3 k $\Omega$  resistors are in series combination are in parallel with a 4.7 k $\Omega$  resistor. What will be the voltage across the 4.7 k $\Omega$  resistors if the voltage across one of the 3.3 k $\Omega$  resistors is 12 V


- a) 24 V
- b) 12 V
- c) 0 V
- d) 6 V

---

*Answer: (a) 24 V*

5. Calculate Voltage across 2 $\Omega$  Resistor where supply  $v = 10$  volts.

- a) 2V
- b) 3V
- c) 10V
- d) 4V

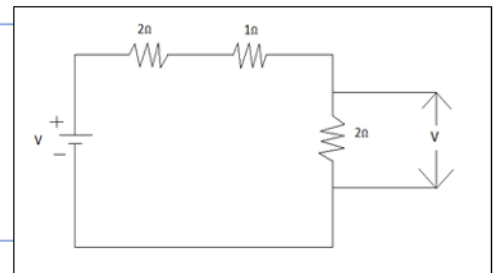

*Answer: d*

*Explanation:  $I = 10/5 = 2A$*

$$V_2 = 10(2)$$


$$V_2 = I \cdot R_2$$

$$= 2(2)$$

$$4V.$$

---

6. Calculate  $i = ?$

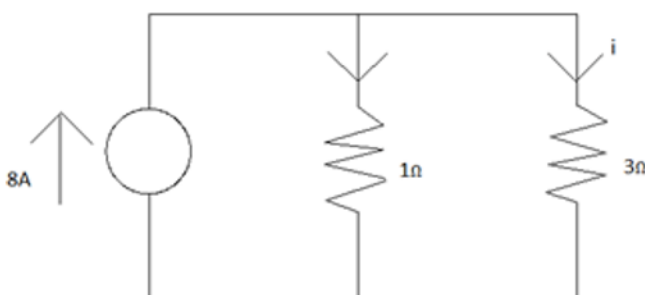



- a) -1A
  - b) +2A
  - c) 8A
  - d) -5A
- 

*Answer: b*

7 For a parallel connected resistor  $R_1$ ,  $R_2$  with total current  $I$  and a voltage of  $V$  volts. Current across the first resistor ( $R_1$ ) is given by

- a)  $I R_1$
  - b)  $I R_2$
  - c)  $I R_1 / R_1 + R_2$
  - d)  $I R_2 / R_1 + R_2$
- 


*Answer: d*

---



## Star Delta Transformation

1. Find the equivalent delta circuit.

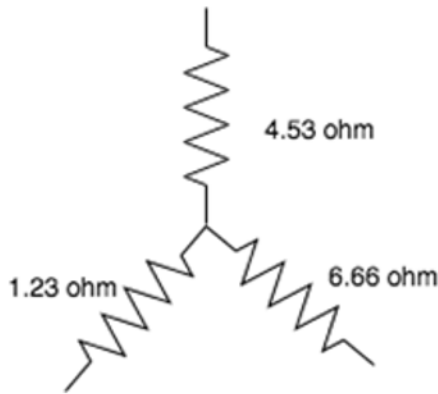

- a) 9.69 ohm, 35.71 ohm, 6.59 ohm  
 b) 10.69 ohm, 35.71 ohm, 6.59 ohm  
 c) 9.69 ohm, 34.71 ohm, 6.59 ohm  
 d) 10.69 ohm, 35.71 ohm, 7.59 ohm

Answer: a

Explanation: Using the star to delta conversion:

$$R1 = 4.53 + 6.66 + 4.53 \times 6.66 / 1.23 = 35.71 \text{ ohm}$$

$$R2 = 4.53 + 1.23 + 4.53 \times 1.23 / 6.66 = 6.59 \text{ ohm}$$

$$R3 = 1.23 + 6.66 + 1.23 \times 6.66 / 4.53 = 9.69 \text{ ohm.}$$


2. Which, among the following is the correct expression for star-delta conversion?

- a)  $R1 = Ra \times Rb / (Ra + Rb + Rc)$ ,  $R2 = Rb \times Rc / (Ra + Rb + Rc)$ ,  $R3 = Rc \times Ra / (Ra + Rb + Rc)$   
 b)  $R1 = Ra / (Ra + Rb + Rc)$ ,  $R2 = Rb / (Ra + Rb + Rc)$ ,  $Rc = / (Ra + Rb + Rc)$   
 c)  $R1 = Ra + Rb + Ra \times Rb / Rc$ ,  $R2 = Rc + Rb + Rc \times Rb / Ra$ ,  $R3 = Ra + Rc + Ra \times Rc / Rb$   
 d)  $R1 = Ra \times Rb / Rc$ ,  $R2 = Rc \times Rb / Ra$ ,  $R3 = Ra \times Rc / Rb$

Answer: c

Explanation: After converting to delta, each delta connected resistance is equal to the sum of the two resistance it is connected to + product of the two resistances divided by the remaining resistance. Hence  $R1 = Ra + Rb + Ra \times Rb / Rc$ ,  $R2 = Rc + Rb + Rc \times Rb / Ra$ ,  $R3 = Ra + Rc + Ra \times Rc / Rb$ .

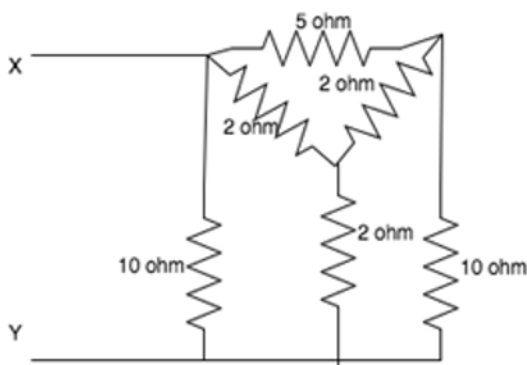3. Find the equivalent resistance between X and Y.



- a) 3.33 ohm  
 b) 4.34 ohm  
 c) 5.65 ohm



d) 2.38 ohm

---

Answer: d

*Explanation: The 3 2ohm resistors are connected in star, changing them to delta, we have  $R1=R2=R3= 2+2+2*2/2=6$  ohm.*

*The 3 6ohm resistors are connected in parallel to the 10 ohm 5 ohm and 10ohm resistors respectively.*

*This network can be further reduced to a network consisting of a 3.75ohm and 2.73ohm resistor connected in series whose resultant is intern connected in parallel to the 3.75 ohm resistor.*

---

4. Delta connection is also known as \_\_\_\_\_

- a) Y-connection
- b) Mesh connection
- c) Either Y-connection or mesh connection
- d) Neither Y-connection nor mesh connection

---

Answer: b

*Explanation: Delta connection is also known as mesh connection because its structure is like a mesh, that is, a closed loop which is planar.*

---

5.  $R_a$  is resistance at A,  $R_b$  is resistance at B,  $R_c$  is resistance at C in star connection. After transforming to delta, what is resistance between B and C?

- a)  $R_c+R_b+R_c*R_b/R_a$
- b)  $R_c+R_b+R_a*R_b/R_c$
- c)  $R_a+R_b+R_a*R_c/R_b$
- d)  $R_c+R_b+R_c*R_a/R_b$

---

Answer: a

*Explanation: After converting to the delta, each delta connected resistance is equal to the sum of the two resistances it is connected to+product of the two resistances divided by the remaining resistance. Hence, resistance between B and C =  $R_c+R_b+R_c*R_b/R_a$ .*

---

6.  $R_a$  is resistance at A,  $R_b$  is resistance at B,  $R_c$  is resistance at C in star connection. After transforming to delta, what is resistance between A and C?

- a)  $R_a+R_b+R_a*R_b/R_c$
- b)  $R_a+R_c+R_a*R_c/R_b$
- c)  $R_a+R_b+R_a*R_c/R_a$
- d)  $R_a+R_c+R_a*R_b/R_c$

---

Answer: b

*Explanation: After converting to the delta, each delta connected resistance is equal to the sum of the two resistances it is connected to+product of the two resistances divided by the remaining resistance. Hence, resistance between A and C =  $R_a+R_c+R_a*R_c/R_b$ .*

---



7.  $R_a$  is resistance at A,  $R_b$  is resistance at B,  $R_c$  is resistance at C in star connection. After transforming to delta, what is resistance between A and B?

- a)  $R_c + R_b + R_a \cdot R_b / R_c$
- b)  $R_a + R_b + R_a \cdot R_c / R_b$
- c)  $R_a + R_b + R_a \cdot R_b / R_c$
- d)  $R_a + R_c + R_a \cdot R_c / R_b$

---

*Answer: c*

*Explanation: After converting to the delta, each delta connected resistance is equal to the sum of the two resistances it is connected to + product of the two resistances divided by the remaining resistance. Hence, resistance between A and B =  $R_a + R_b + R_a \cdot R_b / R_c$ .*

---

8. If a 1ohm 2ohm and 32/3ohm resistor is connected in star, find the equivalent delta connection.

- a) 34 ohm, 18.67 ohm, 3.19 ohm
- b) 33 ohm, 18.67 ohm, 3.19 ohm
- c) 33 ohm, 19.67 ohm, 3.19 ohm
- d) 34 ohm, 19.67 ohm, 3.19 ohm

---

*Answer: a*

*Explanation: Using the formula for delta to star conversion:  
Using the formula for delta to star conversion:*

$$R_1 = 1 + 2 + 1 \cdot 2 / (32/3)$$

$$R_2 = 1 + 32/3 + 1 \cdot (32/3) / 2$$

$$R_3 = 2 + 32/3 + 2 \cdot (32/3) / 1.$$

---

9. If an 8/9ohm, 4/3ohm and 2/3ohm resistor is connected in star, find its delta equivalent.

- a) 4ohm, 3ohm, 2ohm
- b) 1ohm, 3ohm, 2ohm
- c) 4ohm, 1ohm, 2ohm
- d) 4ohm, 3ohm, 1ohm

---

*Answer: a*

*Explanation: Using the formula for the star to delta conversion:*


$$R_1 = 8/9 + 4/3 + (8/9) \cdot (4/3) / (2/3)$$

$$R_2 = 8/9 + 2/3 + (8/9) \cdot (2/3) / (4/3)$$

$$R_3 = 2/3 + 4/3 + (2/3) \cdot (4/3) / (8/9).$$

---

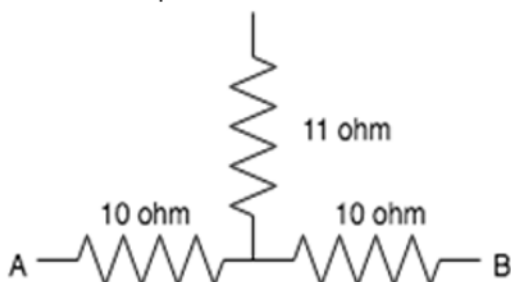10. Find the equivalent resistance between A and B.



- a) 32ohm
- b) 31ohm



- c) 30ohm
- d) 29ohm

---

Answer: d

Explanation: The equivalent resistance between node 1 and node 3 in the star connected circuit is  $R = (10 \times 10 + 10 \times 11 + 11 \times 10) / 11 = 29 \text{ohm}$ .

---

## Kirchhoff's Laws

1. KCL is based on the fact that
  - a) There is a possibility for a node to store energy.
  - b) There cannot be an accumulation of charge at a node.
  - c) Charge accumulation is possible at node
  - d) Charge accumulation may or may not be possible.


---

Answer: b

Explanation: Since the node is not a circuit element, any charge which enters node must leave immediately.

---

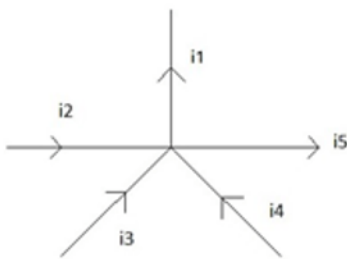2. Relation between currents according to KCL is



- a)  $i_1 = i_2 = i_3 = i_4 = i_5$
- b)  $i_1 + i_4 + i_3 = i_5 + i_2$
- c)  $i_1 - i_5 = i_2 - i_3 - i_4$
- d)  $i_1 + i_5 = i_2 + i_3 + i_4$

---

Answer: d

Explanation: According to KCL, entering currents = leaving currents.

---

3. The algebraic sum of voltages around any closed path in a network is equal to \_\_\_\_\_
  - a) Infinity
  - b) 1
  - c) 0
  - d) Negative polarity

---


Answer: c

Explanation: According to KVL, the sum of voltages around the closed path in a network is zero

---




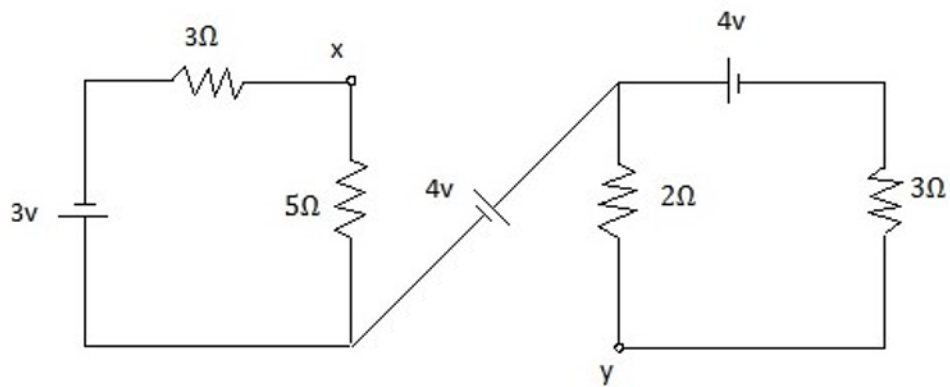4. Calculate potential difference between x and y



- a) 4.275v
- b) -4.275v
- c) 4.527v
- d) -4.527v

Answer: b  
Explanation:

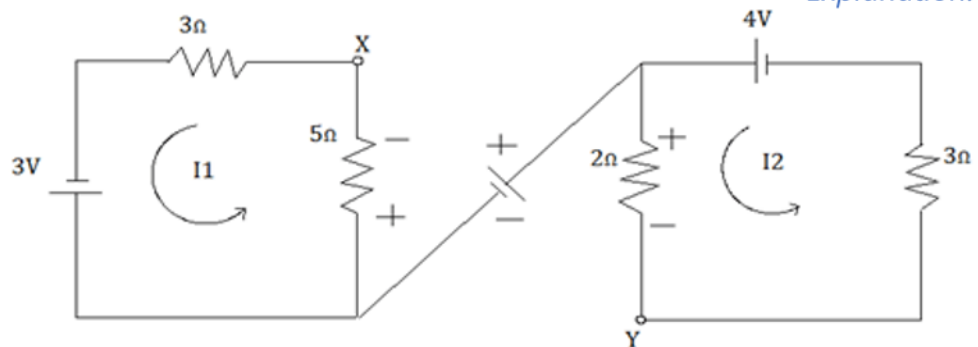

$$I_1 = 3/(3+5) = 3/8 = 0.375\text{A}$$


$$I_2 = 4/5 = 0.8\text{A}$$

$$V_{xy} = V_x - V_y$$

$$V_x + 5I_1 + 4 - 2I_2 - V_y = 0$$

$$V_x - V_y = 2I_2 - 4 - 5I_1 = -4.275\text{V}$$


5. Find R-value from the below circuit?

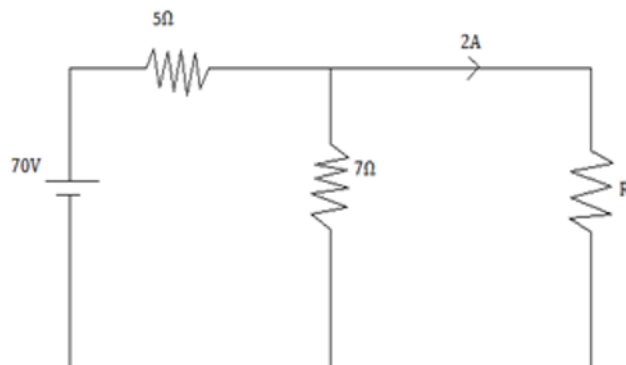

- a) 17.5 Ω
- b) 17.2 Ω
- c) 17.4 Ω
- d) 17.8 Ω



Answer: a  
Explanation:

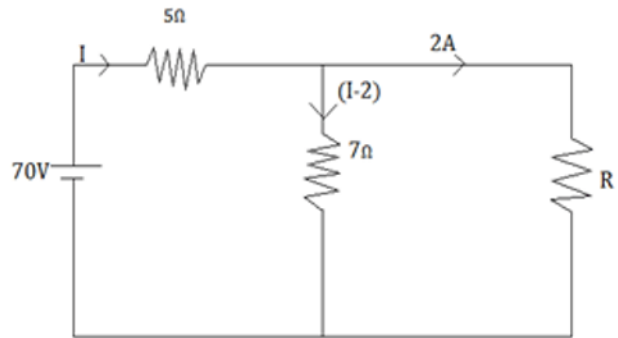


$$\text{KVL: } 70 - 5I - 7(I - 2) = 0$$

$$I = 7\text{A}$$

$$\text{KVL to 2nd loop: } 7(I - 2) - 2R = 0$$


$$R = 17.5\Omega$$

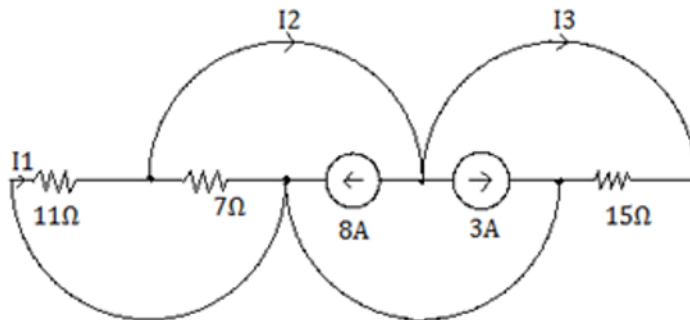6. Determine currents  $I_1$ ,  $I_2$  and  $I_3$ .



- a) -3.3A, -8.5A, 2.4A
- b) 3A, -8A, 2A
- c) 3.3A, 8.5A, -2.4A
- d) 3.2A, 8.6A, 2.3A

Answer: c  
Explanation:

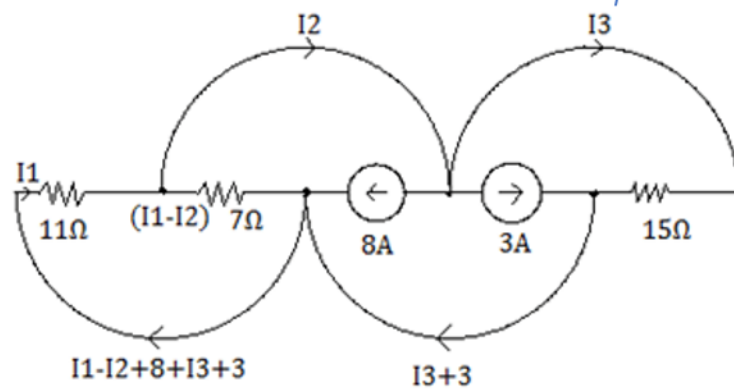

$$I_1 = I_1 - I_2 + 8 + I_3 + 3$$

$$I_2 - I_3 = 11 \dots\dots\dots 1$$

$$\text{And } -11 I_1 - 7(I_1 - I_2) = 0$$

$$-18 I_1 + 7 I_2 = 0 \dots\dots\dots 2$$



And  $-11 I_1 - 15 I_3 = 0$  ..... 3  
Solving  $I_1 = 3.32A$   $I_2 = 8.5A$   $I_3 = -2.4A$ .

---

7. All \_\_\_\_\_ are loops but \_\_\_\_\_ are not meshes

- a) Loops, Meshes
- b) Meshes, loops
- c) Branches, loops
- d) Nodes, Branches


---

Answer: b

Explanation: A mesh cannot be divided further in loops.

---

8. Solve and find the value of I.

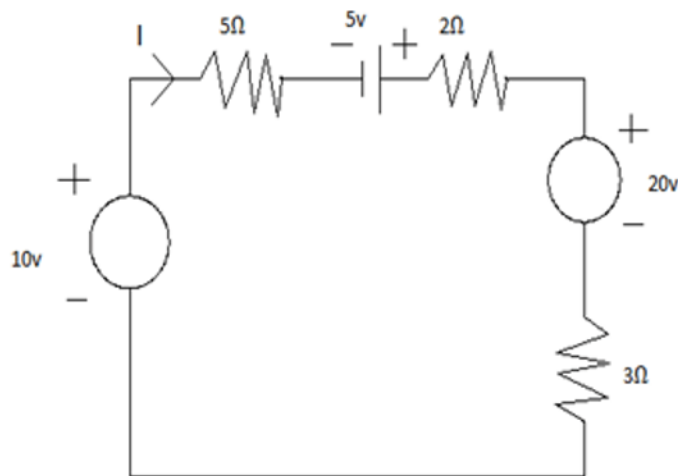

- a) -0.5A
- b) 0.5A
- c) -0.2A
- d) 0.2A

---

Answer: a

Explanation:  $V_{eq} = 10 + 5 - 20 = -5V$

$R_{eq} = 5 + 2 + 3 = 10\Omega$

$I = V/R = -5/10 = -0.5A$ .

---

9. The basic laws for analyzing an electric circuit are :-

- a) Einstein's theory
- b) Newton's laws
- c) Kirchhoff's laws
- d) Faraday's laws

---

Answer: c

Explanation: Kirchhoff's laws are used for analyzing an electric circuit.

---



10. A junction where two (or) more than two network elements meet is known as a

- 
- a) Node
  - b) Branch
  - c) Loop
  - d) Mesh
- 

*Answer: a*

*Explanation: Node is a junction where two or more than two network elements meet.*

---